



INDRAPRASTHA INSTITUTE *of*
INFORMATION TECHNOLOGY
DELHI

Department
of
Electronics & Communication Engineering

Circuit Theory and Devices

Dr. Shobha Sundar Ram

Lab_2: LPF and BPF design in LTSpice

Student Name

Aditya Raj Jain - 2022037

Arnav Shukla - 2022103

Ayushman - 2022128

Date: 23 August 2023

Objective:

As we observed in the previous lab, the transmitter in the SONAR consists of a crystal oscillator that generates a 2MHz sinusoidal signal, and further using a frequency divider a 40KHz (fo) ultrasonic output signal is generated. A low pass filter is used to remove any higher order harmonics that may be generated in processing the signal on the transmitter side. Similarly on the receiver side, the received signal is amplified using a low noise amplifier and passed through a band pass filter to remove higher order harmonics and limit external interference. The filter on the transmitter side may be designed as an active filter to provide voltage amplification to the transmitted signal. The order of a filter is determined by the number of storage elements (capacitors and inductors). The first order LPF filters are series inductor or shunt capacitors.

Theoretical Calculations:

First order active low pass filter \Rightarrow

$$f_A = \frac{1}{2\pi RC}$$

here $f_c = 40 \text{ kHz}$

$$\Rightarrow R = 10 \text{ k}\Omega$$

$$C = 0.3 \text{ nF}$$

Second order active low pass filter \Rightarrow

$$f_L = \frac{1}{2\pi \sqrt{R_3 C_1 R_4 C_2}}$$

$$R_3 = R_4 = 10 \text{ k}\Omega$$

$$C_1 = C_2 = 0.3 \text{ nF}$$

$$f_L = 20 \text{ kHz}$$

First order Band Pass Filter \Rightarrow

$$f_L = \frac{1}{2\pi R_L C_L} = 45 \text{ kHz}$$

$$R_L = 10 \text{ k}\Omega$$

$$C_L = 0.355 \text{ nF}$$

$$f_H = \frac{1}{2\pi R_H C_H} = 35 \text{ kHz}$$

$$R_H = 10 \text{ k}\Omega$$

$$C_H = 0.455 \text{ nF}$$

$$\therefore \text{Bandwidth} = 45 - 35 = \boxed{10 \text{ kHz}}$$

Second order Band Pass filter \Rightarrow

$$f_L = \frac{1}{2\pi R_L C_L}$$

$$= 45 \text{ kHz}$$

$$R_L = 10 \text{ k}$$

$$C_L = 0.355 \text{ n}$$

$$f_H = \frac{1}{2\pi \sqrt{R_{H1} C_{H1} R_{H2} C_{H2}}}$$

$$= 35 \text{ kHz}$$

$$R_{H1} = R_{H2} = 10 \text{ k}$$

$$C_{H1} = \cancel{0.455} = 0.455 \text{ n}$$

$$C_{H2} = 0.4 \text{ n}$$

Edit : $R_1 = 10 \text{ k}$, $R_2 = 40 \text{ k}$, $C_1 = 100 \text{ nF}$, $C_2 = 100 \text{ nF}$

Observations:

First Order RC Low Pass Filter (LPF):

1. **Magnitude Response:** As the frequency increases, the magnitude of the filter response decreases gradually. The roll-off of the filter's magnitude response is observed in the Bode plot.
2. **Phase Response:** The phase response of the first-order LPF changes as the frequency increases. At low frequencies, the phase shift increases as the frequency approaches the cutoff frequency.

Second Order RC Low Pass Filter (LPF):

1. **Magnitude Response:** The second-order LPF has a steeper roll-off compared to the first-order LPF.
2. **Phase Response:** Like the first-order LPF, the phase response of the second-order LPF changes as the frequency increases. The steeper roll-off is reflected in the phase response as well.



First Order RC Band Pass Filter (BPF):


1. **Magnitude Response:** The magnitude response of the first-order BPF shows a peak around the center frequency. This peak corresponds to the passband of the filter, allowing frequencies within the specified bandwidth to pass through.
2. **Phase Response:** The phase response of the first-order BPF varies around the center frequency.


Second Order RC Band Pass Filter (BPF):

1. **Magnitude Response:** The second-order BPF exhibits a narrower and more defined peak in the magnitude response compared to the first-order BPF.
2. **Phase Response:** The phase response of the second-order BPF also shows more defined changes around the center frequency.

Plots:

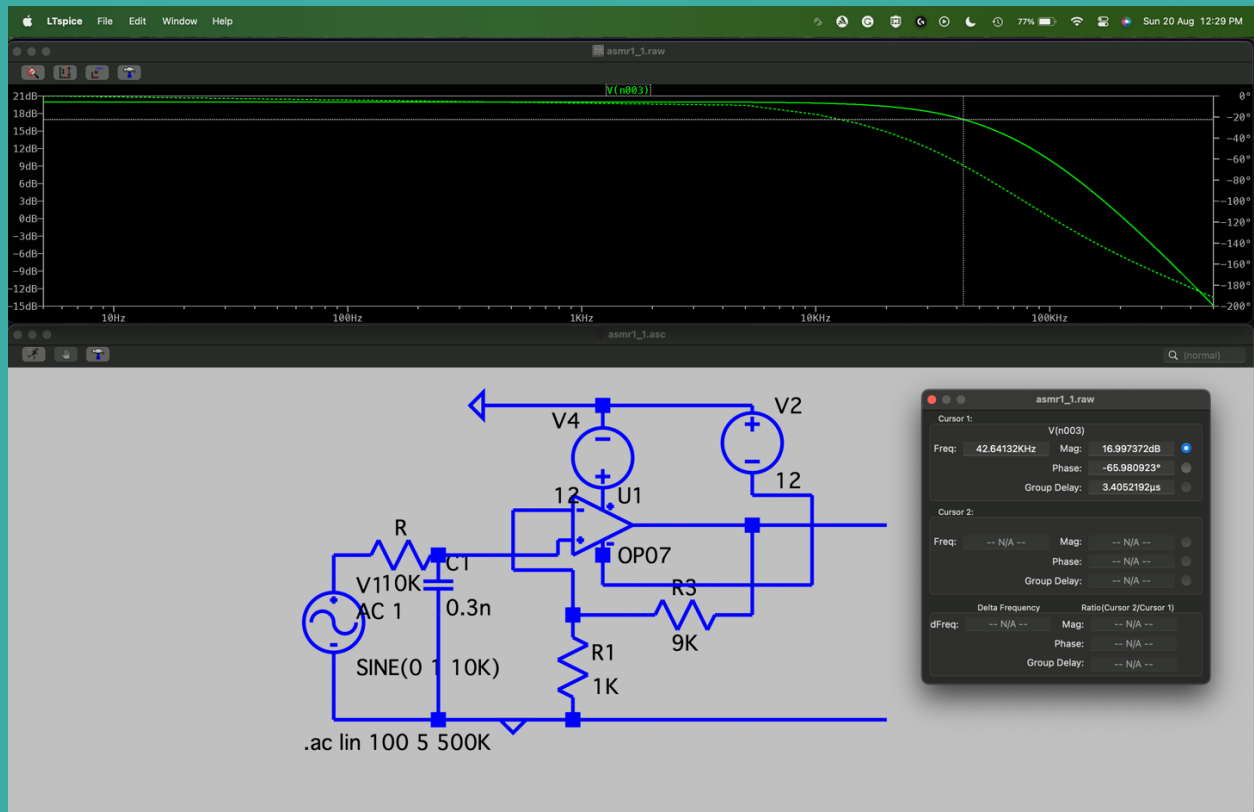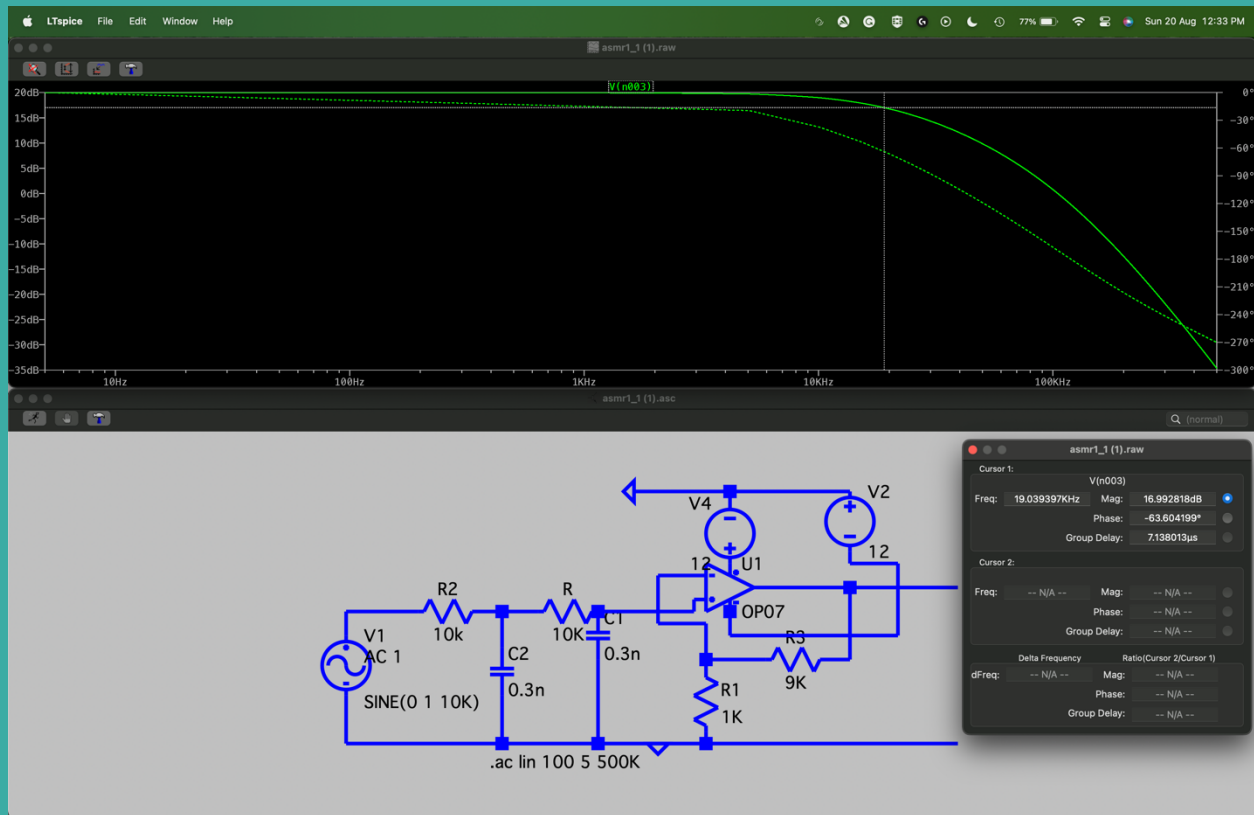

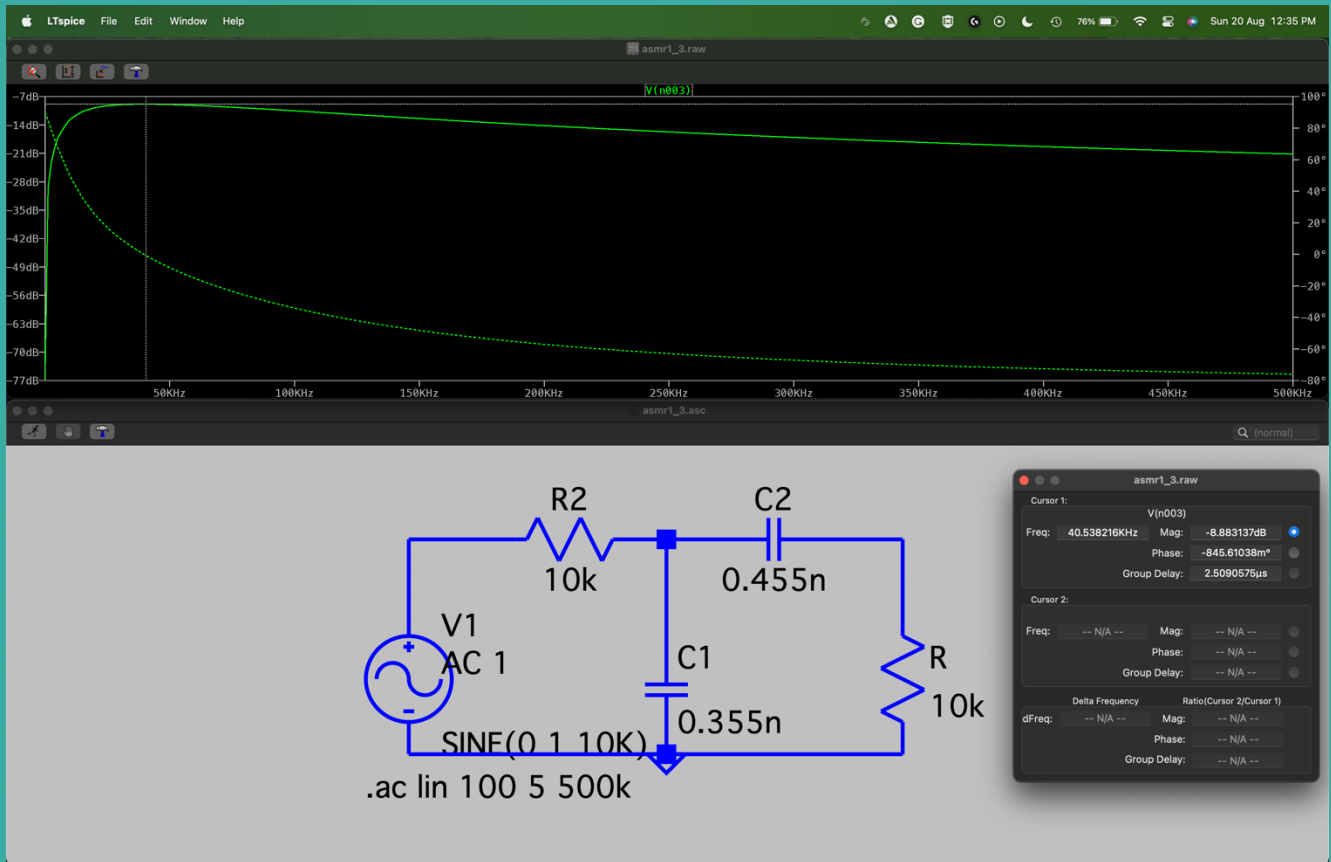

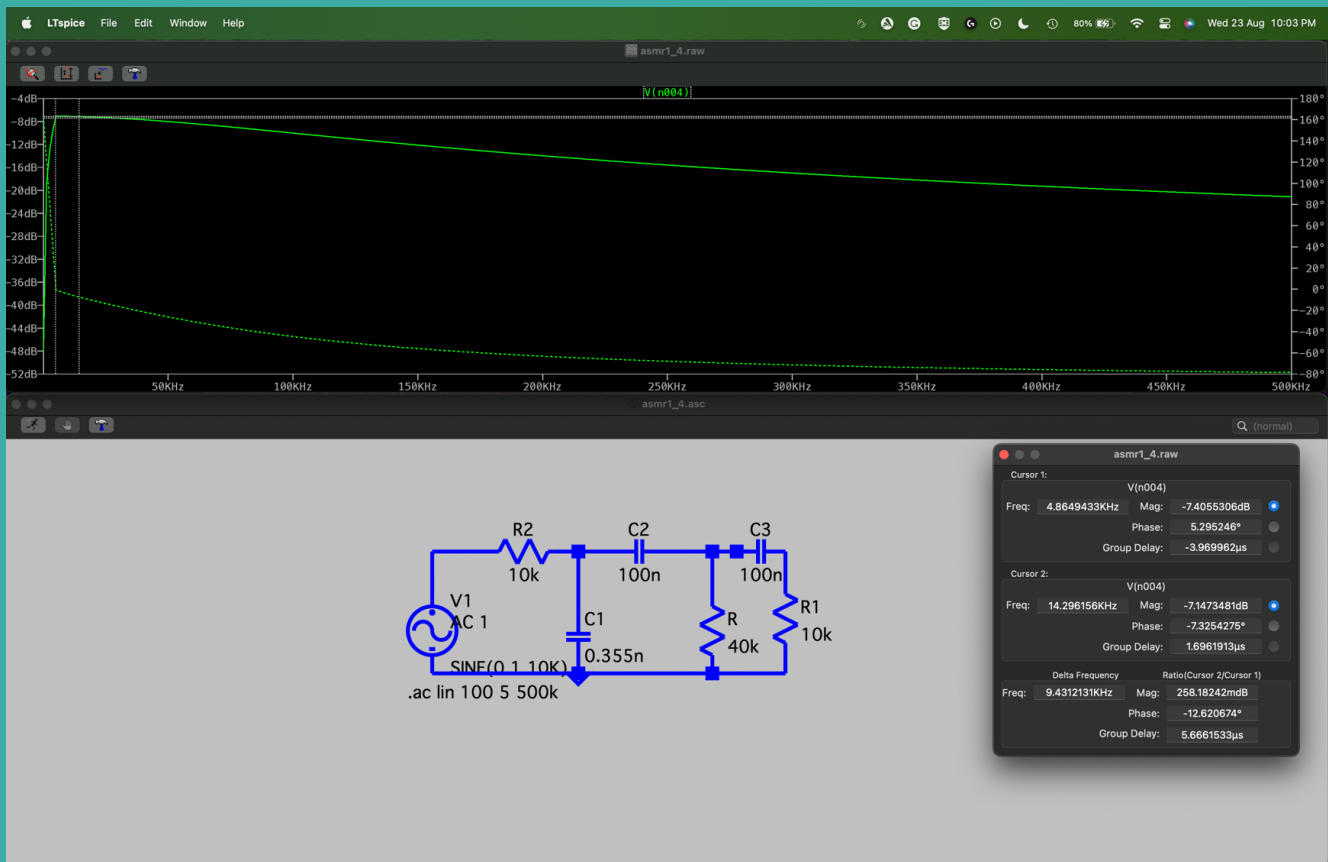

Conclusions:

1. **Frequency Response:** Filters exhibit different frequency responses based on their order and type. Low pass filters allow low frequencies to pass while attenuating high frequencies. Band pass filters allow a specific range of frequencies to pass.
2. **Magnitude and Phase Responses:** The Bode plots for both magnitude and phase responses provide insights into how filters behave across different frequency ranges. Magnitude response indicates the filter's gain behavior, while the phase response shows the phase shift introduced by the filter.
3. **Higher Order Filters:** Second-order filters exhibit steeper roll-offs and better selectivity compared to first-order filters. This increased selectivity is advantageous in applications where precise frequency control is required.
4. **Cutoff Frequencies:** The cutoff frequencies for the filters were determined by the values of the passive components (resistors and capacitors) used in their designs. Changing these values would result in different cutoff frequencies.